



Faculty of Engineering and Technology – Electrical and Computer Engineering Department


First Semester 2017/2018

ENCS234 – Verilog Assignment

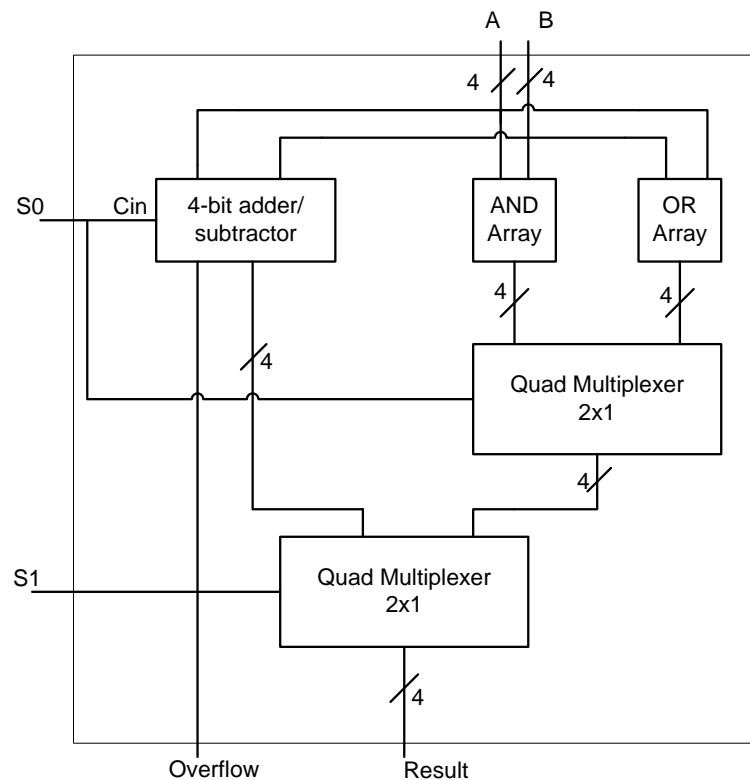**Deadline: 3 (for SMW) or 4 (for TR) /1/2018 (During the class)**

Given the following Combinational circuit, Use Verilog HDL on Quartus tool to

- Implement the 1-bit adder and use it to build 4-bit adder structurally
- Implement the MUX2x1 and then use it to build the Quad MUX 2x1 structurally.
- Implement the 4-bit OR Array
- Implement the 4-bit AND Array
- Use the blocks you implemented in the parts above to build the final system shown in the figure.
- You should show simulation results for each of the above parts



In addition to building the Quartus project, you need to write down one report for **each student** that includes the following items:

1. System Design.
2. Verilog code.
3. Simulation results.

There would be a discussion for each project with date allocated by the instructors.

**Note:** There is no group work